

①

a	b	$c_{in}$	Sum	$c_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$c_{out}$ : MSOP:  $\sum m(3, 5, 6, 7)$

$ab \backslash c_{in}$	0	1
00	0	0
01	0	1
11	1	1
10	0	1

$\Rightarrow ab + bc_{in} + ac_{in}$

Sum: MSOP:  $\sum m(1, 2, 4, 7)$

$ab \backslash c_{in}$	0	1
00	0	1
01	1	0
11	0	1
10	1	0

$\Rightarrow \bar{a}\bar{b}\bar{c}_{in} + a\bar{b}\bar{c}_{in} + \bar{a}b c_{in} + ab c_{in}$

② Sum using XOR

Use 2 XOR:  $x = a \oplus b = \bar{a}b + a\bar{b}$

$$\text{Sum} = x + c_{in} = a \oplus b \oplus c_{in}$$

$$\text{Sum} = \bar{a}\bar{b}c_{in} + \bar{a}b\bar{c}_{in} + ab c_{in} + a\bar{b}\bar{c}_{in}$$

$$= c_{in} (\bar{a}\bar{b} + ab) + \bar{c}_{in} (\bar{a}b + a\bar{b})$$

$$= c_{in} (a \oplus b) + \bar{c}_{in} (a \oplus b)$$

$$= a \oplus b \oplus c_{in}$$

$C_{out}$  implemented NAND-NAND

$$C_{out} = ab + bc_{in} + ac_{in}$$
$$= \overline{(\overline{ab})(\overline{bc_{in}})(\overline{ac_{in}})}$$

③ for a full adder,  $C_{out} = 1$  when at least 2 of 3 inputs ( $a, b, c_{in}$ ) are 1

$$\Rightarrow (a, b, c_{in}) = (0, 1, 1)$$

$$(a, b, c_{in}) = (1, 0, 1)$$


$$(a, b, c_{in}) = (1, 1, 0)$$




$$(a, b, c_{in}) = (1, 1, 1)$$

$$Sum = a \oplus b \oplus c_{in}$$


$$\Rightarrow C_{out} = ab + c_{in}(a \oplus b)$$
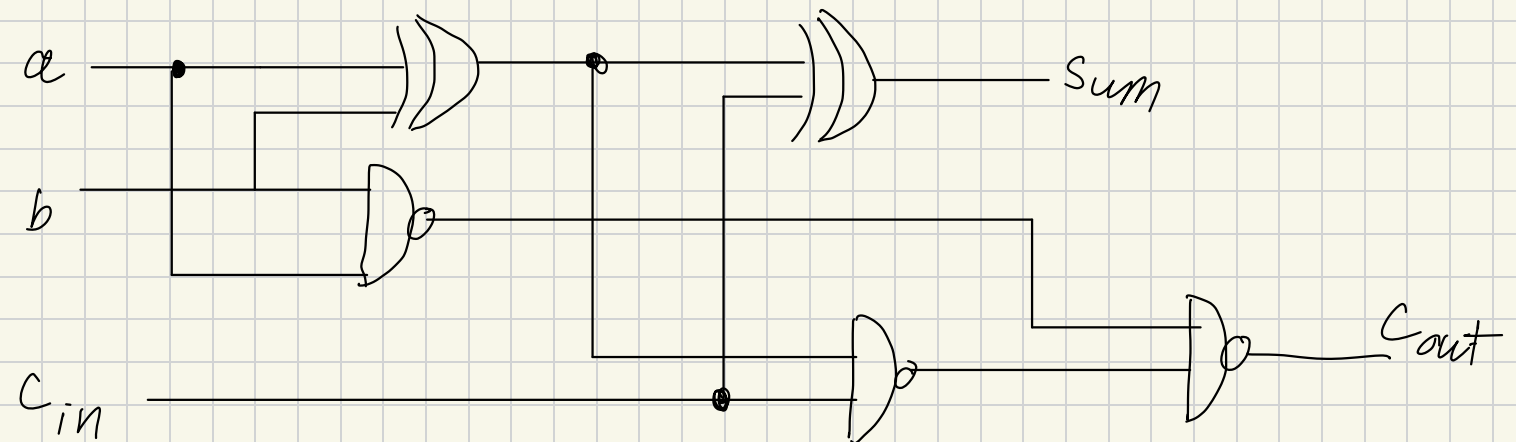
$$= ab + c_{in}(\bar{a}b + a\bar{b})$$
$$= \overline{(\overline{ab})(\overline{a \oplus b c_{in}})}$$



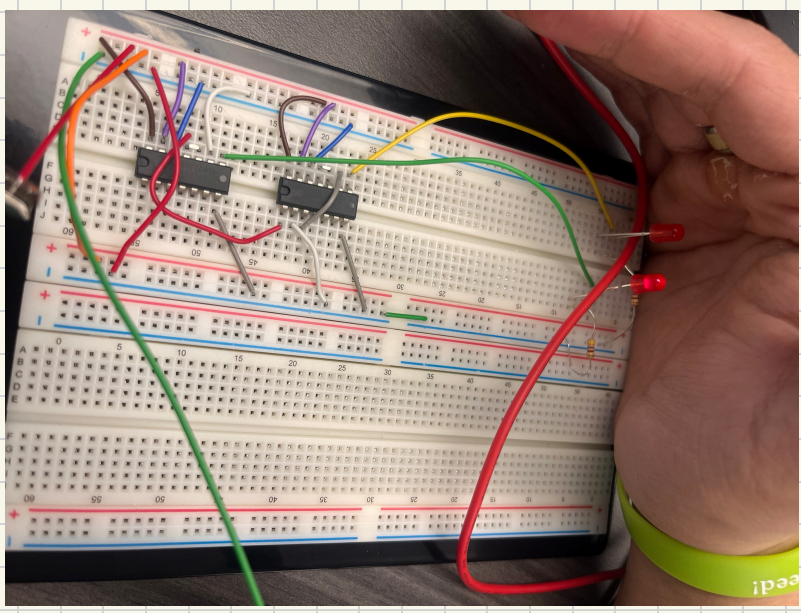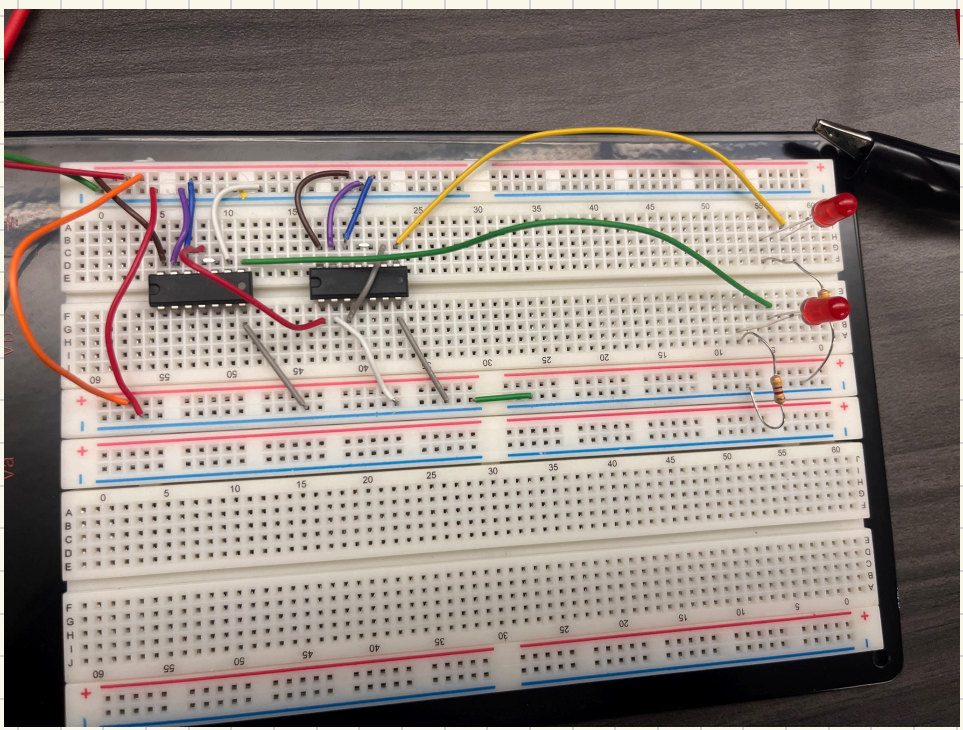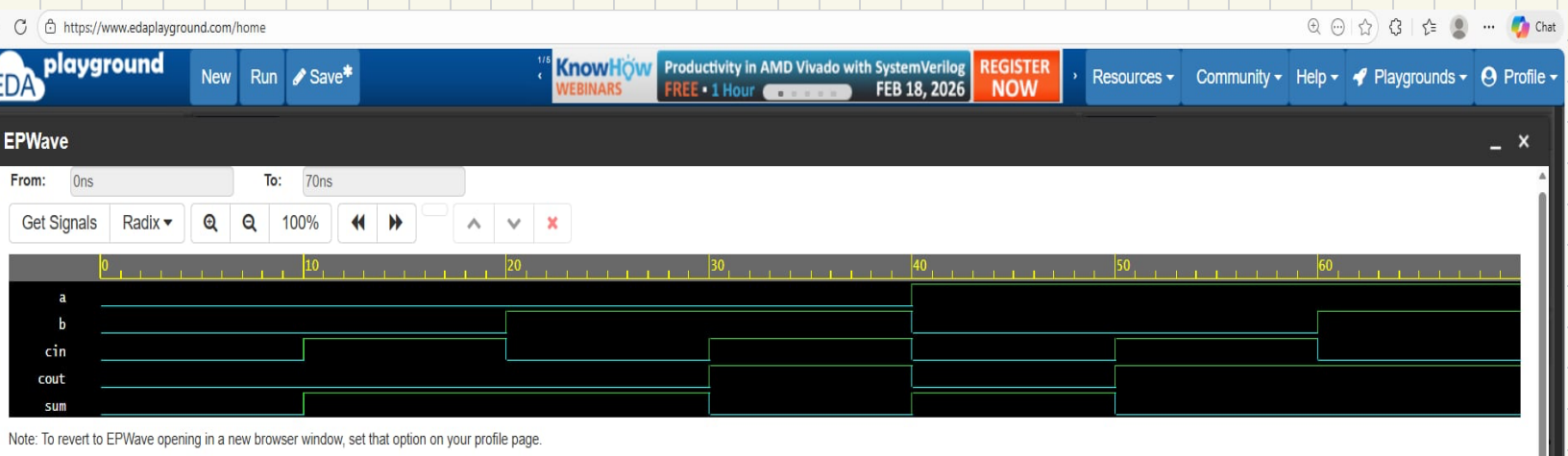

$$a = 1, b = 0, cin = 0$$

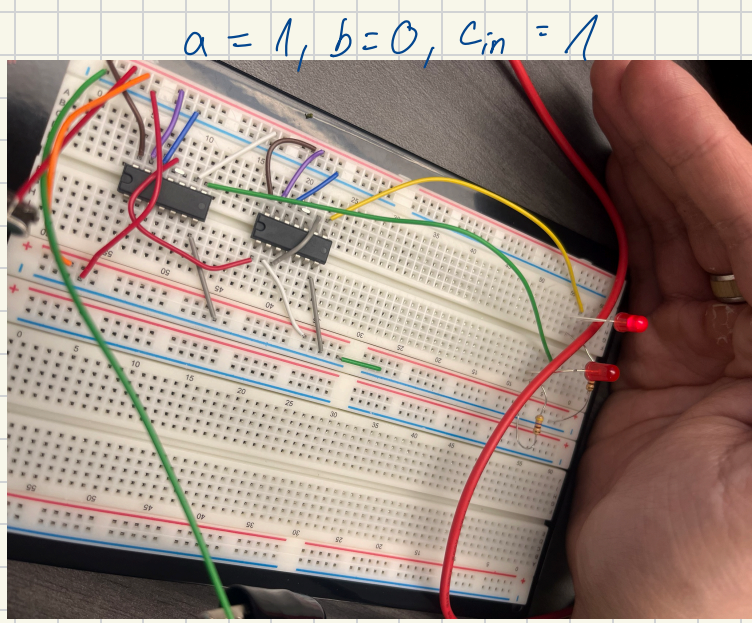

$$a = 1, b = 0, cin = 1$$